

Lab 6: Design & Characterization of a Flop-Flop

ECEN 454-503

Alexia Perez, 127008512


Purpose: This lab serves to further students' knowledge of creating schematics, layouts, and post-layout simulations. It also introduces a new concept, setup time, and teaches students how to measure it.


Procedure:

- 1) Create a Flip-Flop schematic based on that given in the lab manual. Check and save.
- 2) Create a layout for this Flip-Flop that matches the schematic, and run DRC. If DRC passes, run LVS. If LVS passes, create the post-layout schematic.
- 3) Vary the load at the output to find the rising and falling delays of the Flip-Flop. Ensure that the rising and falling delays have a difference less than 10% when the load is 100fF.
- 4) Use a sinusoidal voltage source and run an ac analysis of the circuit to measure input capacitance.
- 5) Vary the delay time of the input to the Flip-Flop, and record the delay of the last signal that went through the Flip-Flop without reaching a meta-stable state. Repeat this process to find the falling setup time as well.

Results:

 - 1) The schematic and layout are displayed below. The schematic is based off of that given in the lab manual, and there were no problems creating this circuit. However, creating the layout took much longer, as many proximity issues came up in the DRC originally. Those issues were fixed, and the LVS passed.



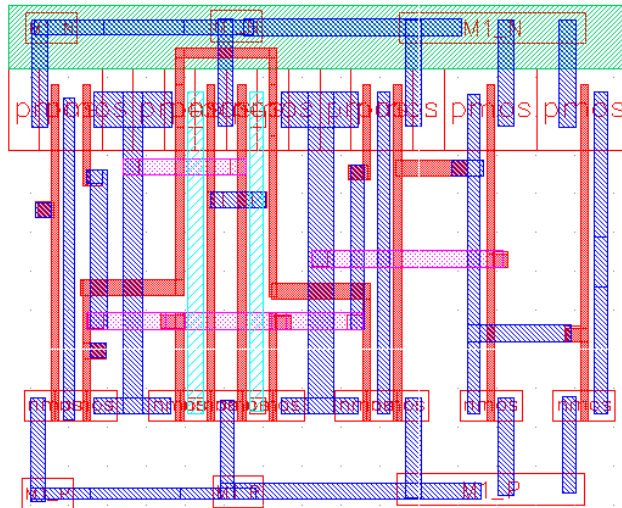

Below are the DRC and LVS results from the schematic and layout.

```
DRC started.....Wed Oct 20 20:40:18 2021
  completed ....Wed Oct 20 20:40:18 2021
  CPU TIME = 00:00:00  TOTAL TIME = 00:00:00
  ***** Summary of rule violations for cell "FlipFlop layout" *****
  Total errors found: 0
```

Compiling Diva LVS rules...

```
Net-list summary for /home/ugrads/a/alexia_perezv/cadence/LVS/layout/netlist
count
13      nets
6        terminals
10      pmos
10      nmos
```

```
Net-list summary for /home/ugrads/a/alexia_perezv/cadence/LVS/schematic/netlist
count
13      nets
6        terminals
10      pmos
10      nmos
```


```
Terminal correspondence points
N9      N3      CLK
N7      N1      GND
N11     N12     IN
N8      N0      OUT
N12     N10     VDD
N10     N5      ~CLK
```

```
Devices in the netlist but not in the rules:
pcapacitor
```

```
Devices in the rules but not in the netlist:
cap nfet pfet nmos4 pmos4
```

The net-lists match.

 
- 2) Below is the first plot saved to verify correctness of the design. It can be seen that the input propagates to the output only on the rising edge of the clock. This simulation was done with a 100fF load.



- 3) Below is a table displaying the recorded rising & falling clock-to-Q delays. As it can be seen, at 100fF the error difference between rising and falling delay is ~10%, but as the load capacitance decreases, this error increases.


Capacitance	Rising Delay	Falling Delay	Error
100fF	0.73 ns	0.65 ns	10.96%
90fF	0.68 ns	0.6 ns	11.76%
70fF	0.6 ns	0.51 ns	15%
50fF	0.51 ns	0.43 ns	15.69%
40fF	0.46 ns	0.38 ns	17.39%
30fF	0.42 ns	0.34 ns	19.05%
20fF	0.37 ns	0.29 ns	21.62%
10fF	0.33 ns	0.25 ns	24.24%
5fF	0.3 ns	0.22 ns	26.67%
1fF	0.28 ns	0.2 ns	28.57%

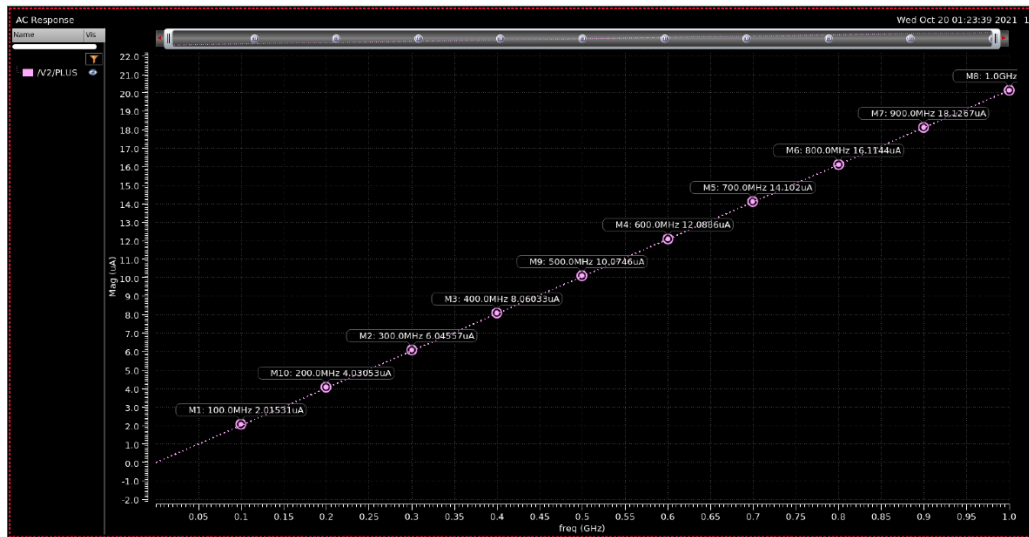- 4) For the sink capacitance measurement, the waveform obtained is displayed below.




To calculate the sink capacitance for each point, the formula $C = I/2\pi f$ was used, and then the 10 results were averaged for an **overall sink capacitance of 3.207fF**.

 - 5) The graphs for the rising and falling setup times are displayed below. For this lab, the parametric simulation method was used to find these values, so as you can see below, there are multiple output signals for the varying input delays.



 The rising setup time was found to be $10\text{ns} - 9.85\text{ns} = 0.15\text{ns}$



The falling setup time was found to be $20\text{ns} - (10\text{ns} + 9.73\text{ns}) = 0.27\text{ns}$.
Thus, the overall setup time is 0.27 ns.

Conclusion: This lab helped the student to further develop their skills in creating schematics, layouts, and post-layout simulations. It also became apparent how the delays of the circuit affect the rising and falling setup time.